
 


計算機結構

(數位邏輯與電子學)

陳鍾誠 於金門大學

邏輯閘

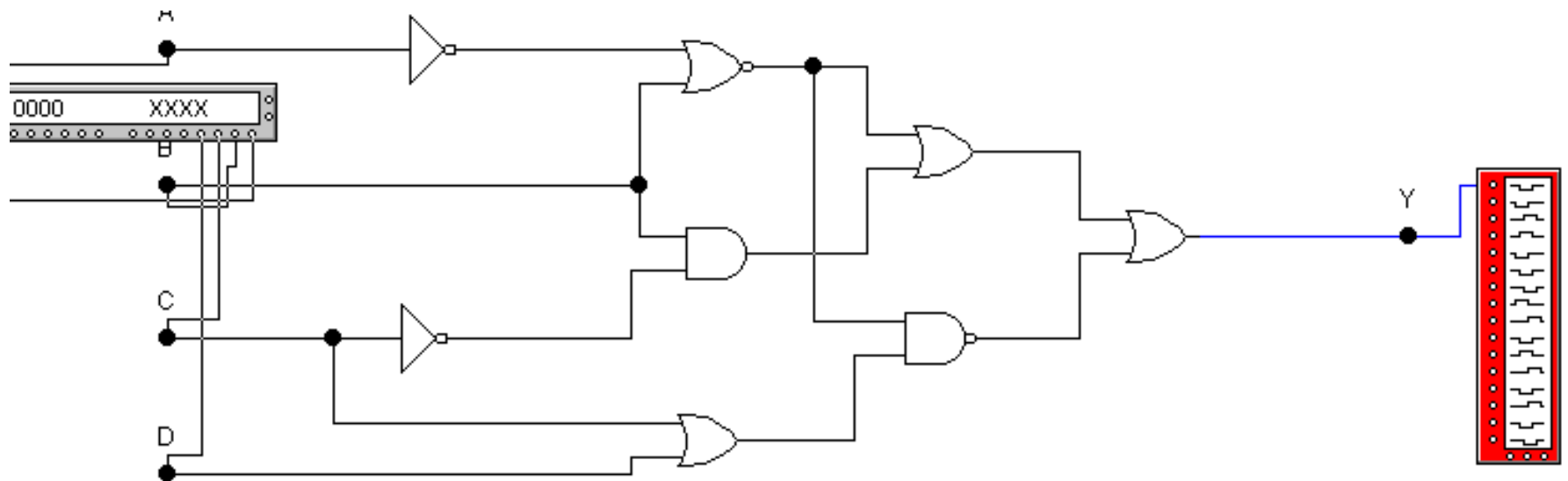

邏輯閘是由電晶體所組成的

- 電晶體

- 類型

- 雙極接面電晶體 (TTL、ECL)
 - 金氧半導體場效電晶體 (MOSFET)




主流


- 特徵

- 某些狀況下、電會流過、某些狀況下不會。
 - 穿遂效應。

MOSFET

 


P-Channel MOSFET : 斷路狀態

 


因為正電對正電排斥，正電進不來，因此不通。

P-Channel MOSFET : 斷路狀態

 



因為正電對正電排斥，正電進不來，因此不通。

P-Channel MOSFET : 通路狀態

 


因為負電吸引下，正電穿過 N 型矽，通了，稱為穿隧效應。


P-Channel v. s. N-Channel

 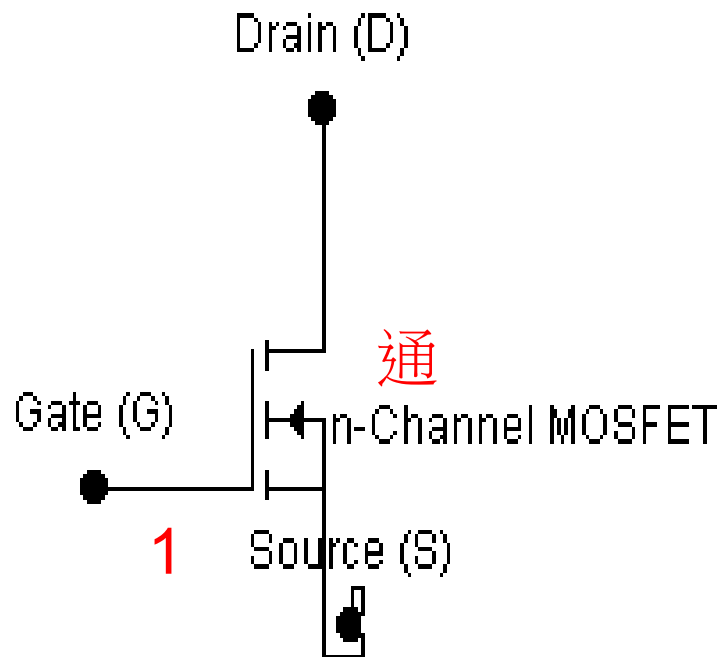

CMOS Inverter (not)

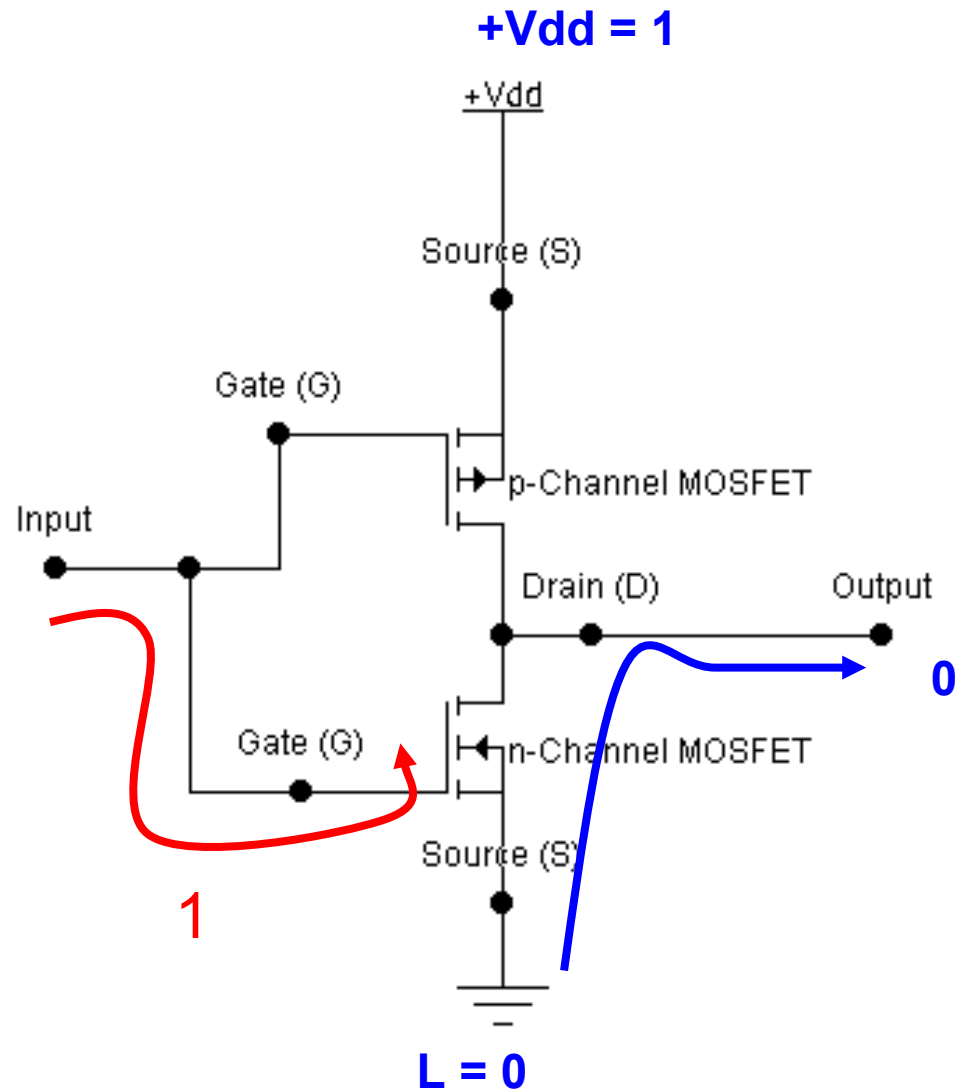


CMOS Inverter (not)

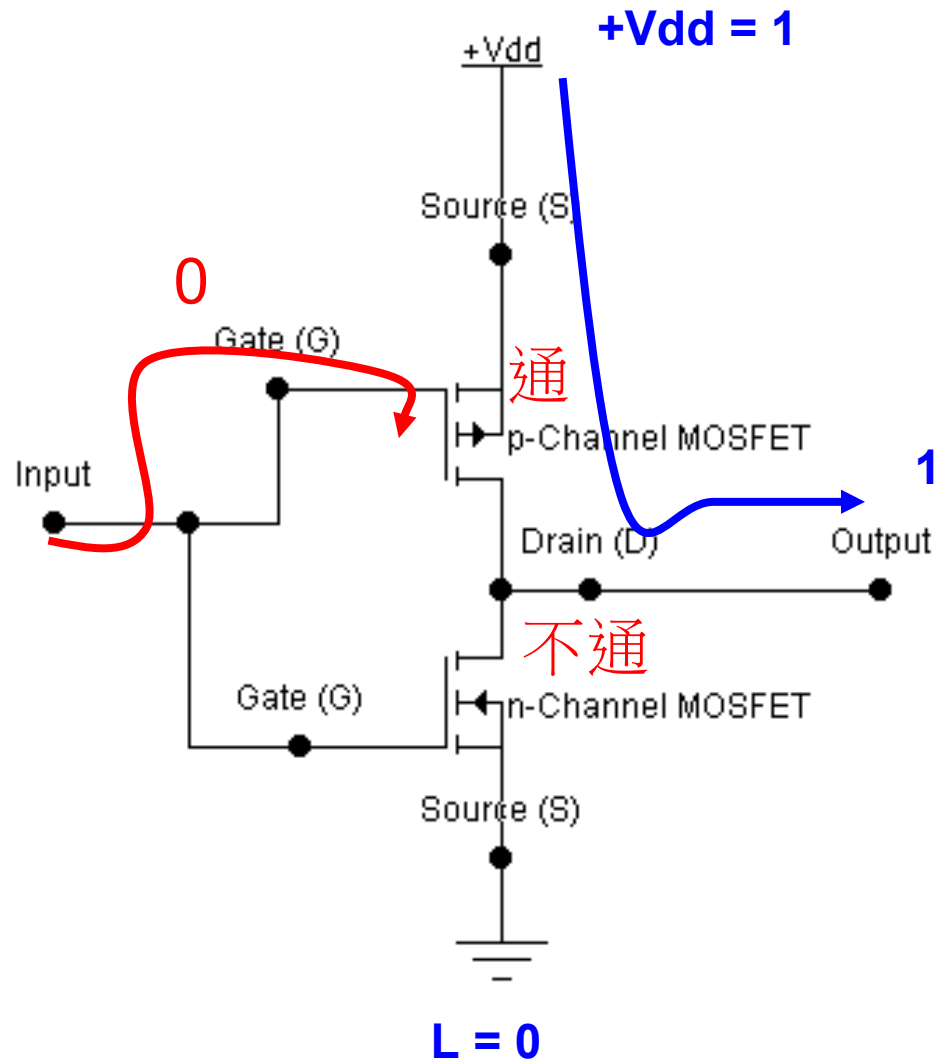

CMOS NAND

$V_{DD}=1$

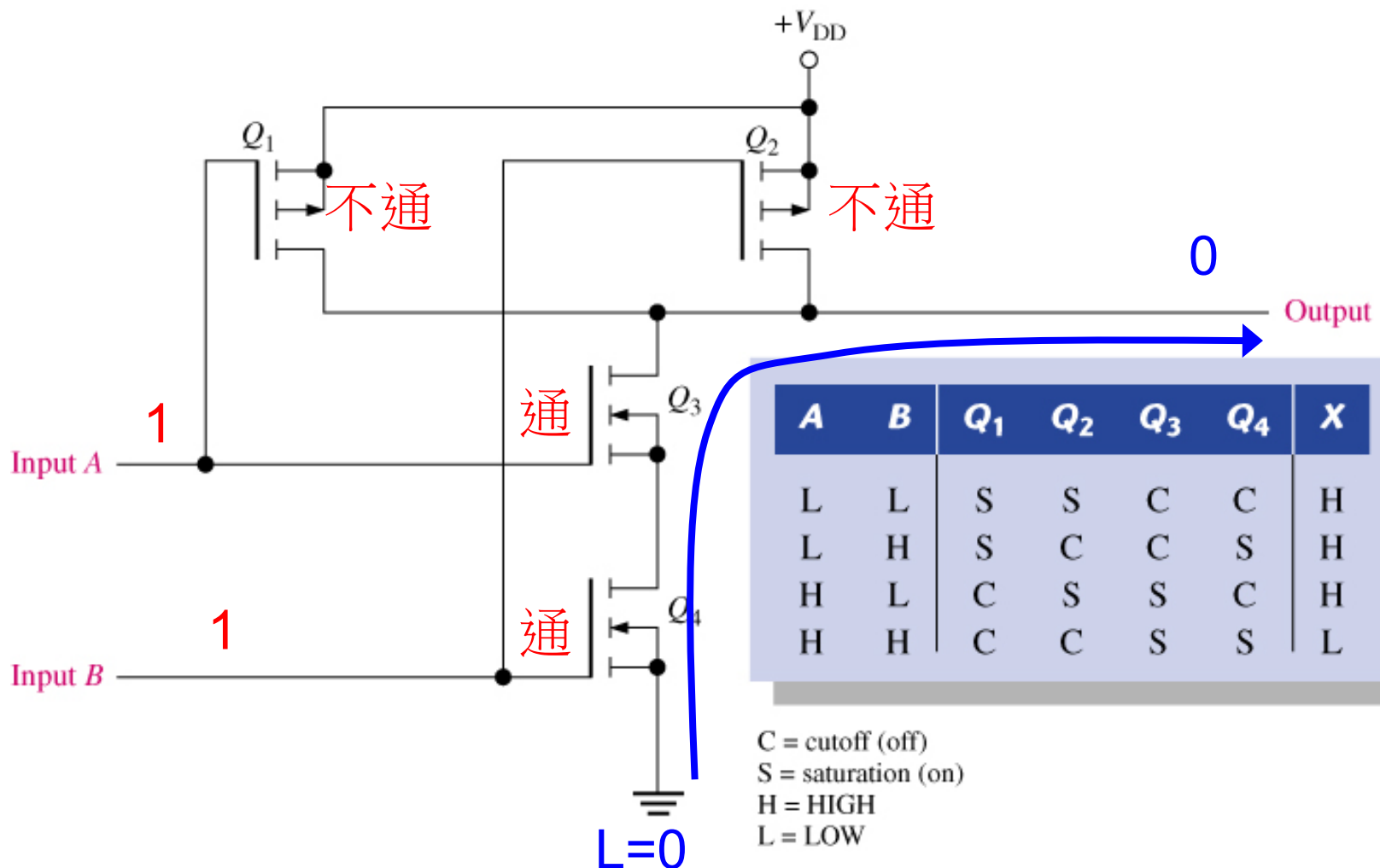

結語

- 資工系的硬體課程都學完了
- 對硬體有興趣的同學請到電子系修電子學與計算機結構！
- 對系統軟體有興趣的同學請修系統程式與作業系統！



程式語言

系統程式

計算機結構

數位邏輯

電子學

半導體材料

計算機結構－邏輯電路的背後

陳鍾誠 於金門大學

邏輯閘


- AND



- OR



- NOT

 

Logic Function Implementation


■ Using Switches

- For inputs:
 - logic 1 is switch closed
 - logic 0 is switch open
- For outputs:
 - logic 1 is light on
 - logic 0 is light off.
- NOT uses a switch such that:
 - logic 1 is switch open
 - logic 0 is switch closed


Switches in parallel => OR



Switches in series => AND

 


Normally-closed switch => NOT

 

Logic Function Implementation (Continued)

- **Example: Logic Using Switches**

 


- Light is on ($L = 1$) for
 $L(A, B, C, D) =$
and off ($L = 0$), otherwise.
- Useful model for relay circuits and for CMOS gate circuits, the foundation of current digital logic technology

Logic Gates

- In the earliest computers, switches were opened and closed by magnetic fields produced by energizing coils in *relays*. The switches in turn opened and closed the current paths.
- Later, *vacuum tubes* that open and close current paths electronically replaced relays.
- Today, *transistors* are used as electronic switches that open and close current paths.
- Optional: Chapter 6 – Part 1: The Design Space


Logic Gate Symbols and Behavior

- Logic gates have special symbols:

 

 (a) Graphic symbols


- And waveform behavior in time as follows:



 (b) Timing diagram

Gate Delay

- In actual physical gates, if one or more input changes causes the output to change, the output change does not occur instantaneously.
- The delay between an input change(s) and the resulting output change is the *gate delay* denoted by t_G :



Logic Diagrams and Expressions


Truth Table

X Y Z	$F = X + \overline{Y} \cdot Z$
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Equation

$$F = X + \overline{Y} Z$$

Logic Diagram

 

- Boolean equations, truth tables and logic diagrams describe the same function!
- Truth tables are unique; expressions and logic diagrams are not. This gives flexibility in implementing functions.


Boolean Algebra

- An algebraic structure defined on a set of at least two elements, B, together with three binary operators (denoted $+$, \cdot and $\overline{}$) that satisfies the following basic identities:

1. $X + 0 = X$	2. $X \cdot 1 = X$	
3. $X + 1 = 1$	4. $X \cdot 0 = 0$	
5. $X + X = X$	6. $X \cdot X = X$	
7. $X + \overline{X} = 1$	8. $X \cdot \overline{X} = 0$	
9. $\overline{\overline{X}} = X$		
<hr/>		
10. $X + Y = Y + X$	11. $XY = YX$	Commutative
12. $(X + Y) + Z = X + (Y + Z)$	13. $(XY)Z = X(YZ)$	Associative
14. $X(Y + Z) = XY + XZ$	15. $X + YZ = (X + Y)(X + Z)$	Distributive
16. $\overline{X + Y} = \overline{X} \cdot \overline{Y}$	17. $\overline{X \cdot Y} = \overline{X} + \overline{Y}$	DeMorgan's

Cost Criteria (continued)

 - Example 1: $\nabla \nabla$ $GN = G + 2 = 9$
- $F = \overset{\bullet}{A} + \overset{\bullet}{B} \overset{\bullet}{C} + \overset{\bullet}{\bar{B}} \overset{\bullet}{\bar{C}}$ $L = 5$
- $G = L + 2 = 7$



- L (literal count) counts the AND inputs and the single literal OR input.
- G (gate input count) adds the remaining OR gate inputs
- GN (gate input count with NOTs) adds the inverter inputs

Cost Criteria (continued)

- **Example 2:**
- $F = A B C + \bar{A}\bar{B}\bar{C}$
- $L = 6 \quad G = 8 \quad GN = 11$
- $F = (A + \bar{C})(\bar{B} + C)(\bar{A} + B)$
- $L = 6 \quad G = 9 \quad GN = 12$
- Same function and same literal cost
- But first circuit has better gate input count and better gate input count with NOTs
- Select it!

