

計算機結構 (數位邏輯基礎)

陳鍾誠 於金門大學

第 4 章

Logic Functions and Gates

Computer Organization and Design Fundamental

書籍作者：David Tarnoff

投影片製作者：陳鍾誠

4.1 Logic Gate Basics


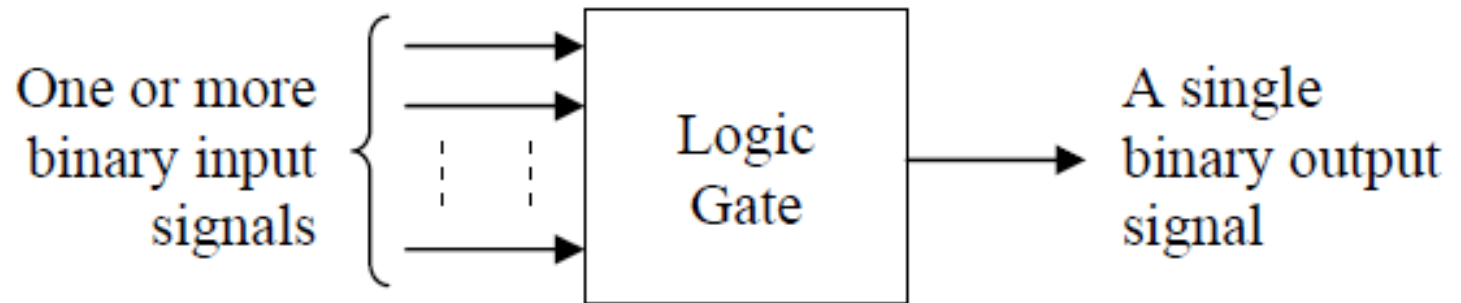


Figure 4-1 Basic Format of a Logic Gate

4 種基本邏輯閘

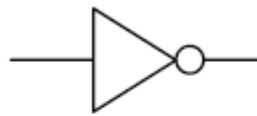

a.) NOT



b.) AND



c.) OR



d.) Exclusive-OR

Figure 4-2 Basic Logic Symbols

4.1.1 NOT Gate (反閘)



Figure 4-3 Operation of the NOT Gate

A	X
0	1
1	0

Figure 4-9 Inverter Truth Table

4.1.2 AND Gate



Figure 4-4 Operation of a Two-Input AND Gate

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

Figure 4-10 Two-Input AND Gate Truth Table

4.1.3 OR Gate

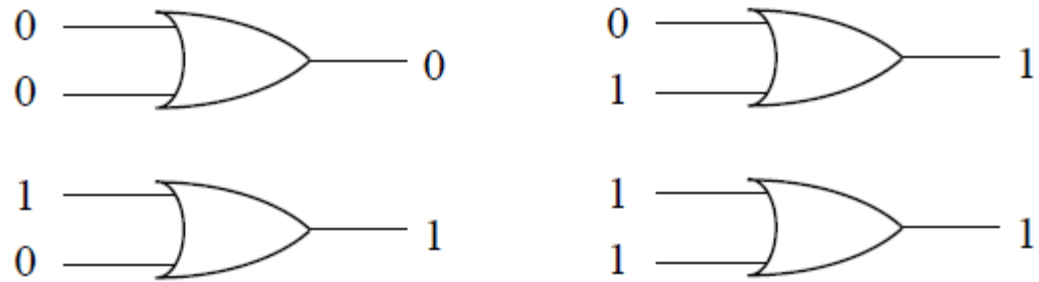


Figure 4-5 Operation of a Two-Input OR Gate

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

Figure 4-11 Two-Input OR Gate Truth Table

4.1.4 Exclusive-OR (XOR) Gate

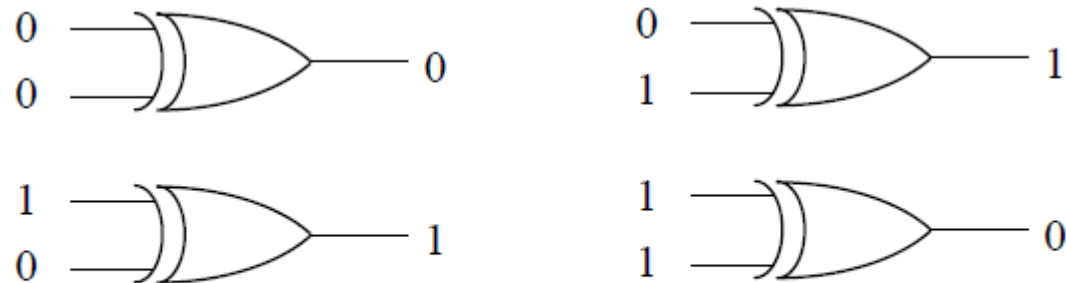


Figure 4-6 Operation of a Two-Input XOR Gate

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

Figure 4-12 Two-Input XOR Gate Truth Table

4.2 Truth Tables (真值表)

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Figure 4-7 Sample Three-Input Truth Table

真值表輸入的完整列舉

A	B	C	D	X
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

Figure 4-8 Listing All Bit Patterns for a Four-Input Truth Table

有 Don't care 的真值表

- X : Don't care, 可以是 0 或 1

A	B	C	X
0	X	X	0
X	0	X	0
X	X	0	0
1	1	1	1

Figure 4-13 Three-Input AND Gate Truth Table With Don't Cares

4.3 Timing Diagrams for Gates

4.3 Timing Diagrams for Gates

三輸入 And 閘的時序圖

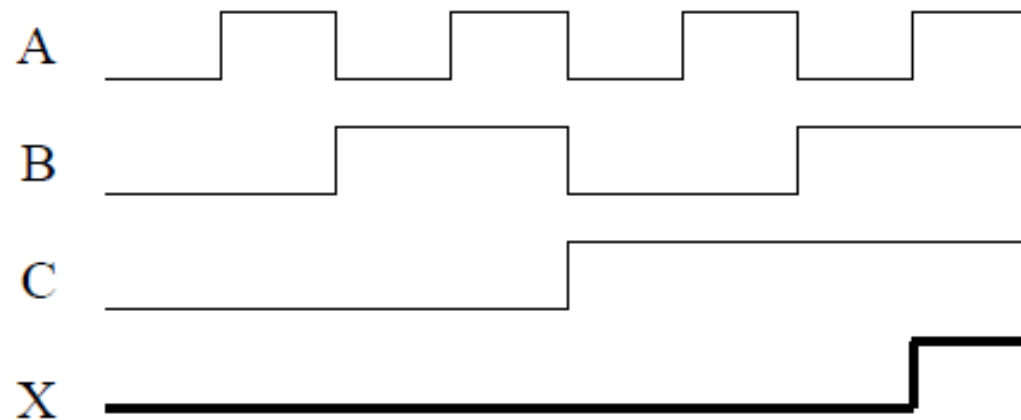


Figure 4-14 Sample Timing Diagram for a Three-Input AND Gate

三輸入 OR 閘的時序圖

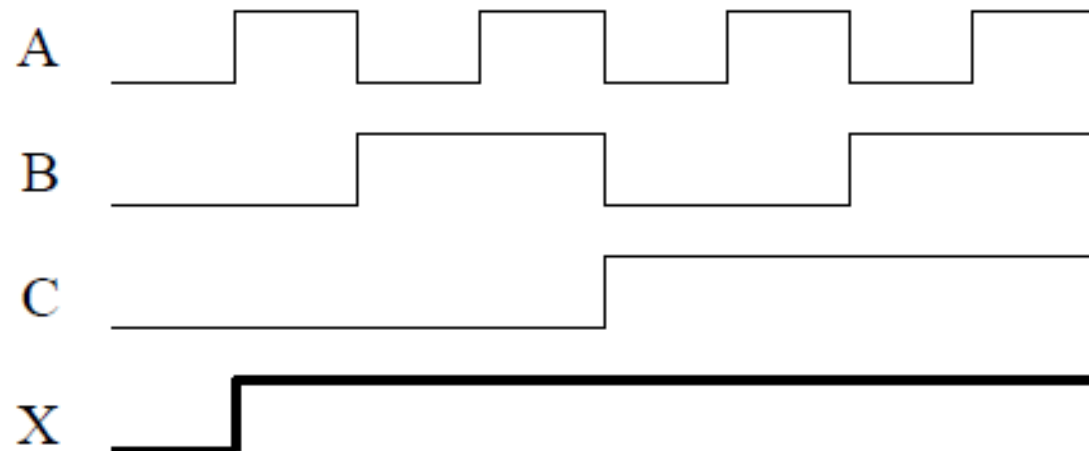


Figure 4-15 Sample Timing Diagram for a Three-Input OR Gate

三輸入 XOR 閘的時序圖

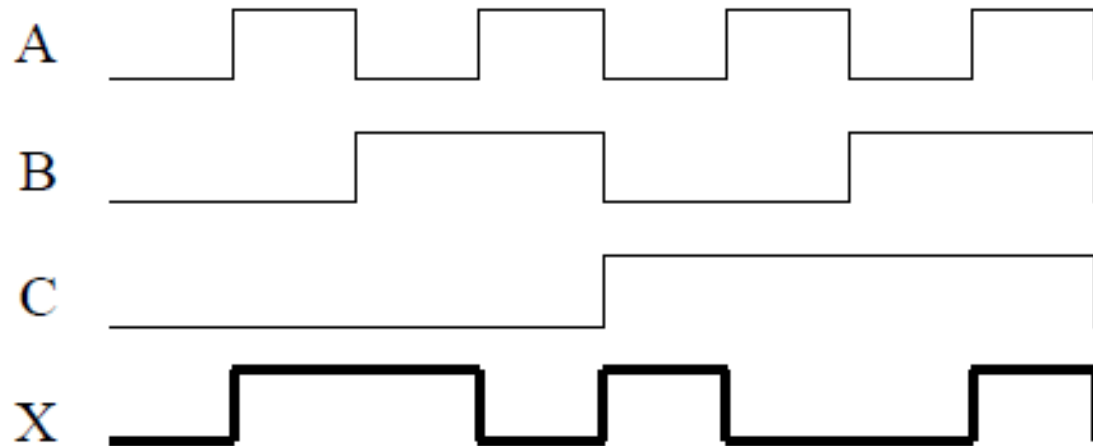


Figure 4-16 Sample Timing Diagram for a Three-Input XOR Gate

4.4 Combinational Logic

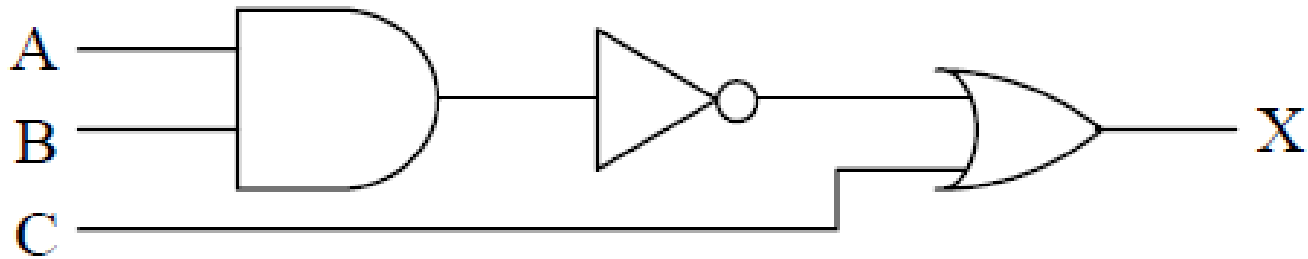


Figure 4-17 Sample Combinational Logic


防盜系統電路

armed

KK [ɑ:md] DJ [ɑ:md]


▶▶即時發音

1. 武裝的, 裝甲的

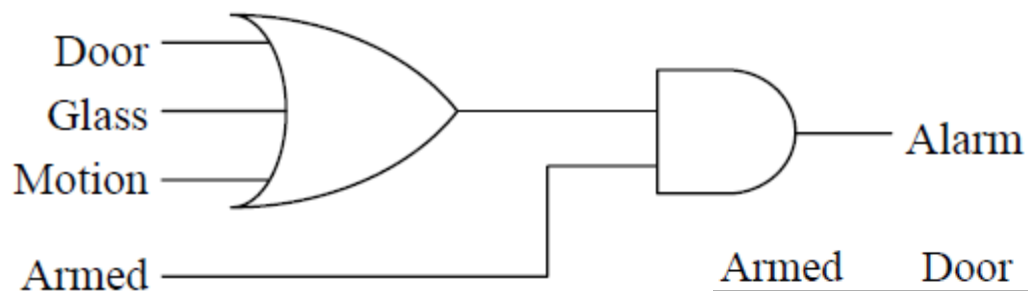


Armed	Door	Glass	Motion	Alarm
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


包含 not 的基本電路符號

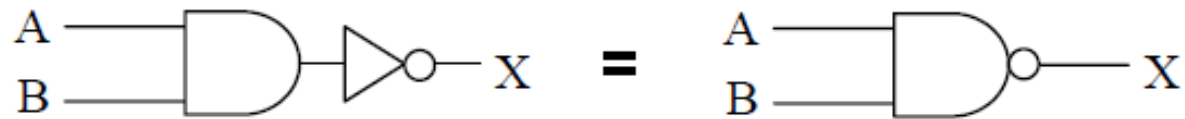

a) AND gate + NOT gate = NAND gate

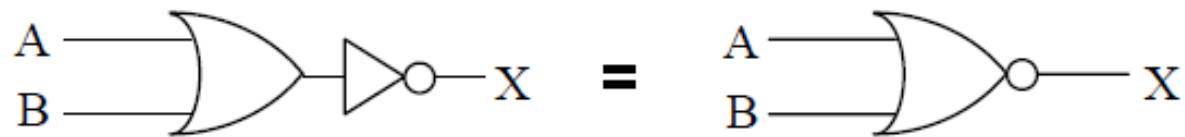

b) OR gate + NOT gate = NOR gate

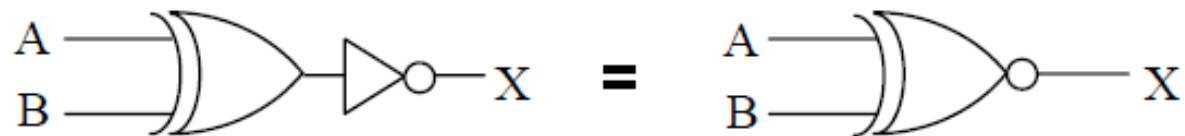

c) Exclusive-OR gate + NOT gate = Exclusive NOR gate

Figure 4-20 "NOT" Circuits

包含 not 的簡化電路圖

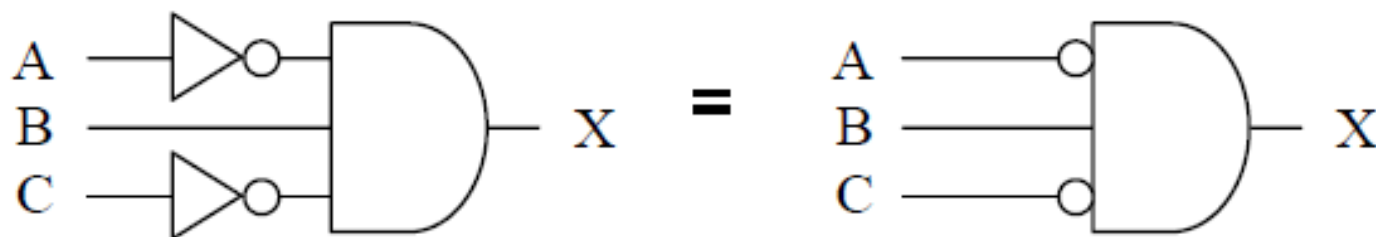


Figure 4-21 Schematic "Short-Hand" for Inverted Inputs

4.5 Truth Tables for Combinational Logic


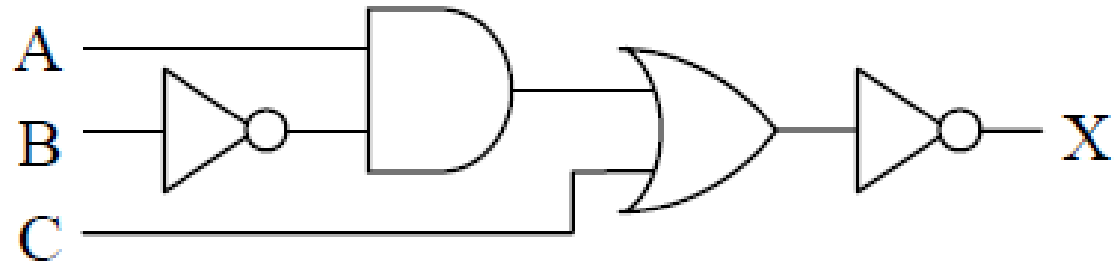



Figure 4-22 Sample of Multi-Level Combinational Logic

如何計算電路的輸出值（單一輸入）

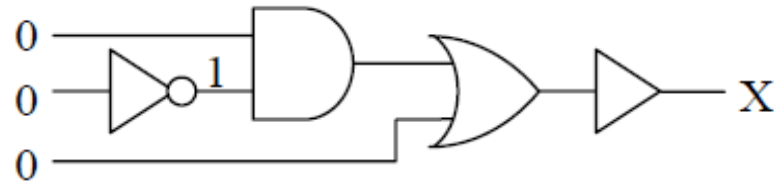
- a.) A 0 is input to the first inverter which outputs a 1.



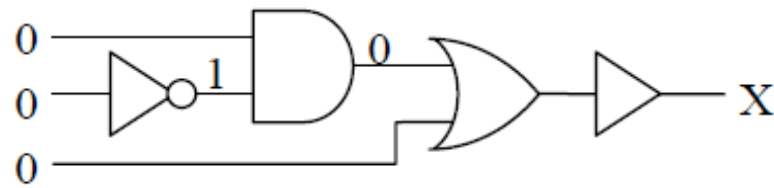- b.) The 1 coming from the inverter is combined with a 0 in the AND gate to output a 0.



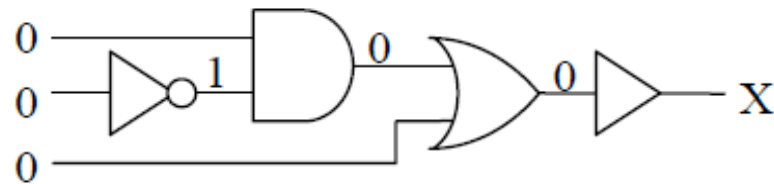- c.) The OR gate receives a 0 from the AND and a 0 from the inputs which makes it output a 0.



- d.) The 0 output from the OR gate passes through the inverter output a 1.


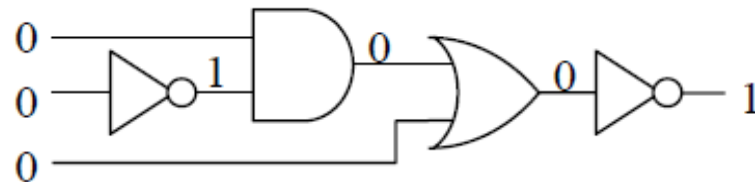


Figure 4-23 Process of Passing Inputs Through Combinational Logic

如何計算電路的輸出值（所有輸入）

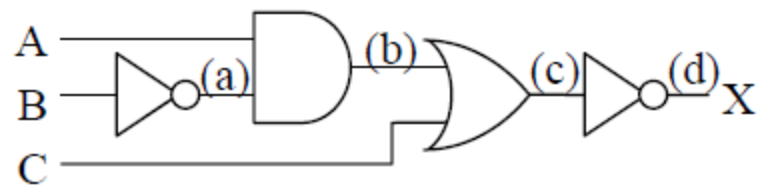

計算 (a)

A	B	C	(a) = NOT of B
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

計算 (b)

A	B	C	(a)	(b)	(c) = (b) OR C
0	0	0	1	0	0
0	0	1	1	0	1
0	1	0	0	0	0
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	0	0	0
1	1	1	0	0	1

計算 (c)

A	B	C	(a)	(b) = (a) AND A
0	0	0	1	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0

計算 (d)


A	B	C	(a)	(b)	(c)	X = (d) = NOT of (c)
0	0	0	1	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	1	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	0	1
1	1	1	0	0	1	0

計算機結構－組合電路

陳鍾誠 於金門大學

同位檢查 (Parity Check) 電路

Hierarchy for Parity Tree Example

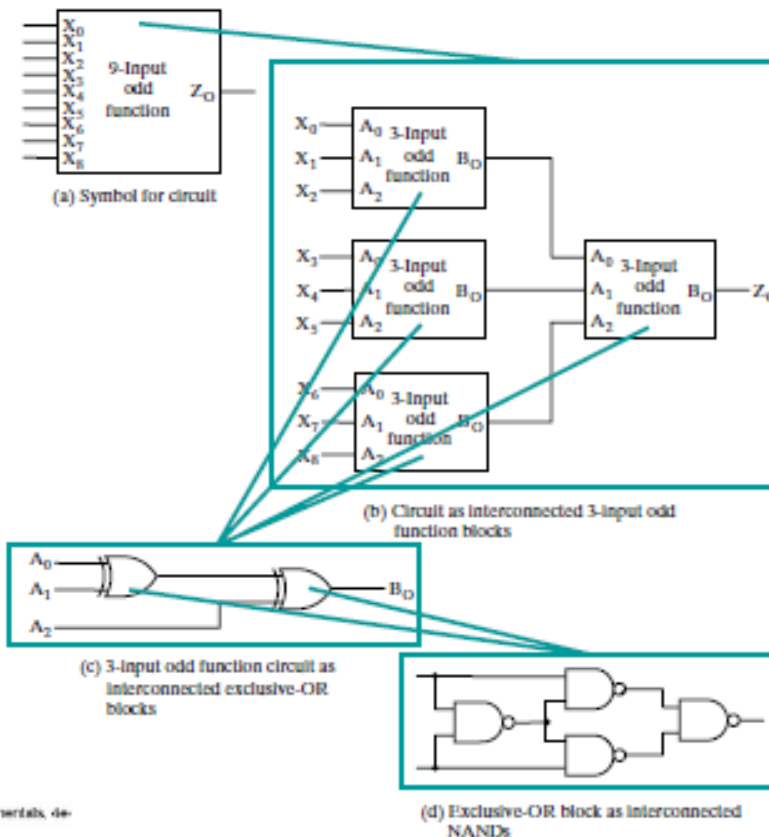


解碼器

Decoder Examples

1-to-2-Line Decoder


A	D ₀	D ₁
0	1	0
1	0	1

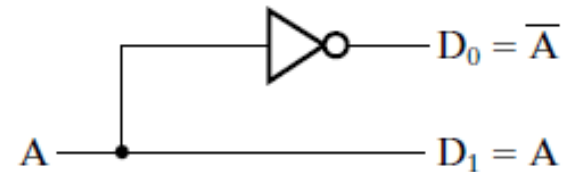

2-to-4-Line Decoder

A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

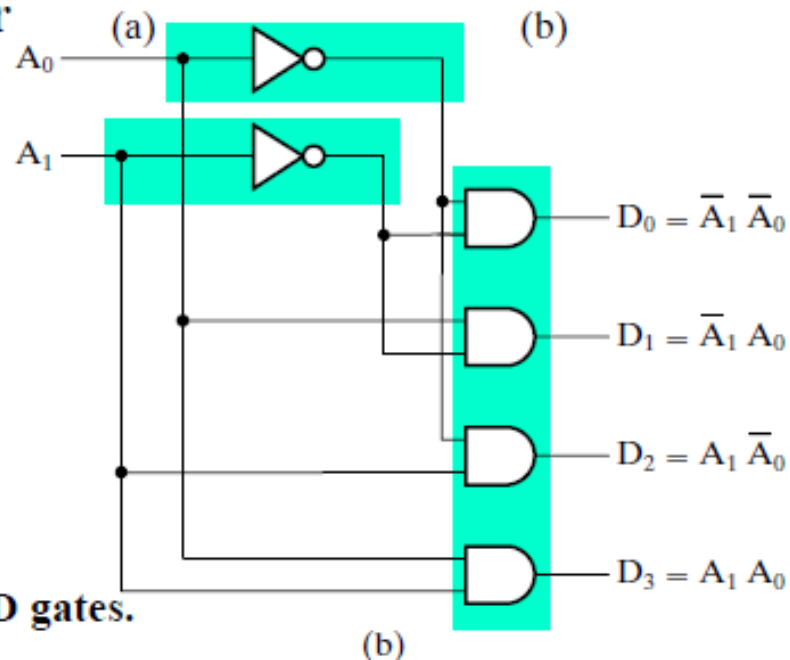


- Note that the 2-4-line made up of 2 1-to-2-line decoders and 4 AND gates.

解碼器的擴展

Decoder Expansion - Example 1

■ Result

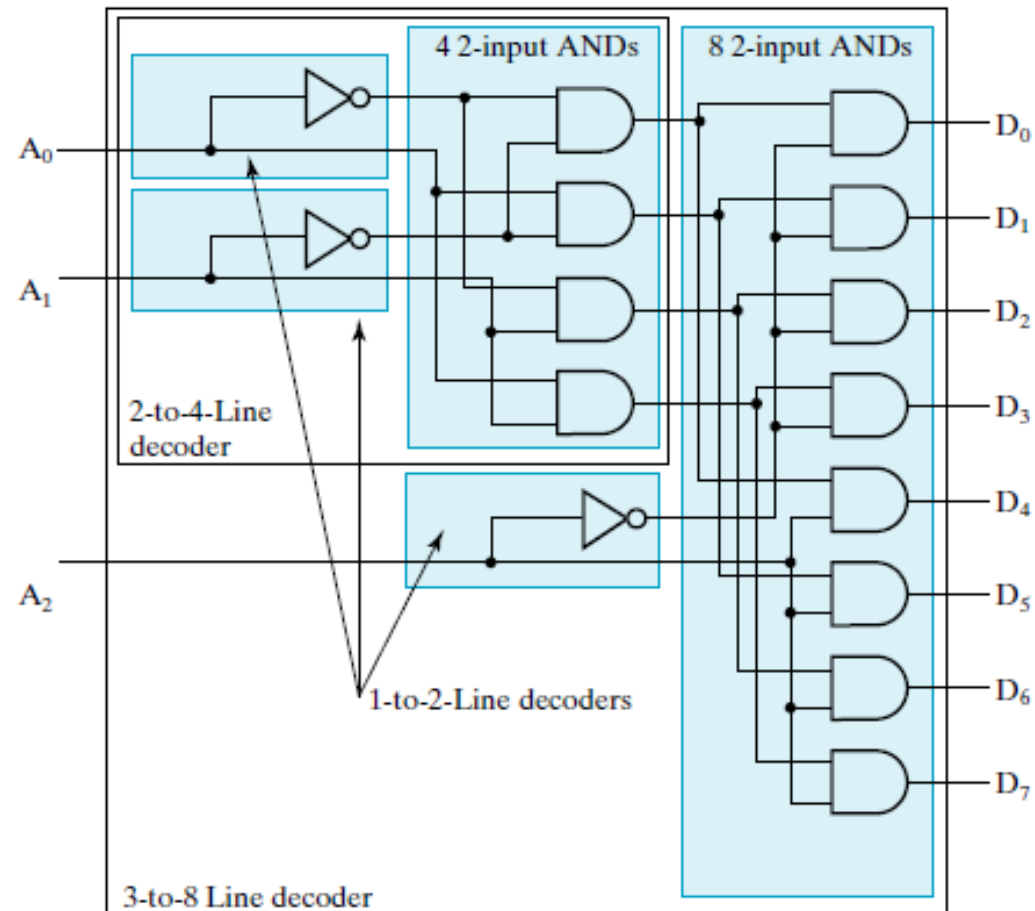


有 Enable 的解碼器

Decoder with Enable

- In general, attach m -enabling circuits to the outputs
- See truth table below for function
 - Note use of X's to denote both 0 and 1
 - Combination containing two X's represent four binary combinations
- Alternatively, can be viewed as distributing value of signal EN to 1 of 4 outputs
- In this case, called a *demultiplexer*

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

(a)

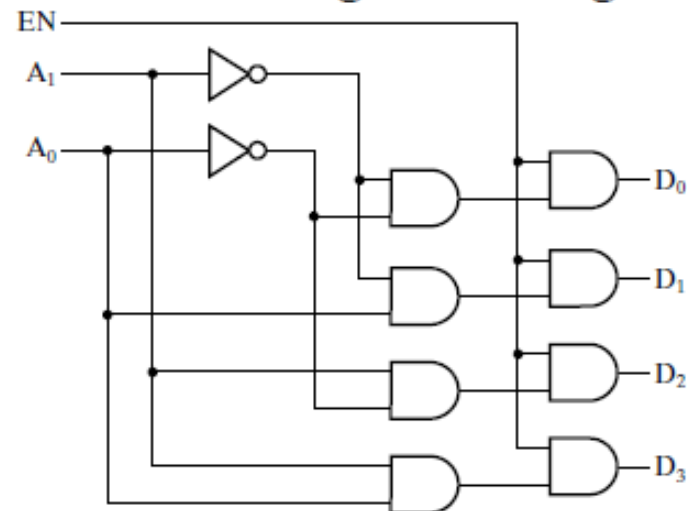

(b)

Priority Encoder Example

- Priority encoder with 5 inputs (D_4, D_3, D_2, D_1, D_0) - highest priority to most significant 1 present - Code outputs A2, A1, A0 and V where V indicates at least one 1 present.

No. of Min-terms/Row	Inputs					Outputs			
	D4	D3	D2	D1	D0	A2	A1	A0	V
1	0	0	0	0	0	X	X	X	0
1	0	0	0	0	1	0	0	0	1
2	0	0	0	1	X	0	0	1	1
4	0	0	1	X	X	0	1	0	1
8	0	1	X	X	X	0	1	1	1
16	1	X	X	X	X	1	0	0	1

- Xs in input part of table represent 0 or 1; thus table entries correspond to product terms instead of minterms. The column on the left shows that all 32 minterms are present in the product terms in the table

2 對 1 多工器


2-to-1-Line Multiplexer

- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - $S = 0$ selects input I_0
 - $S = 1$ selects input I_1

- The equation:

$$Y = \bar{S}I_0 + SI_1$$


- The circuit:

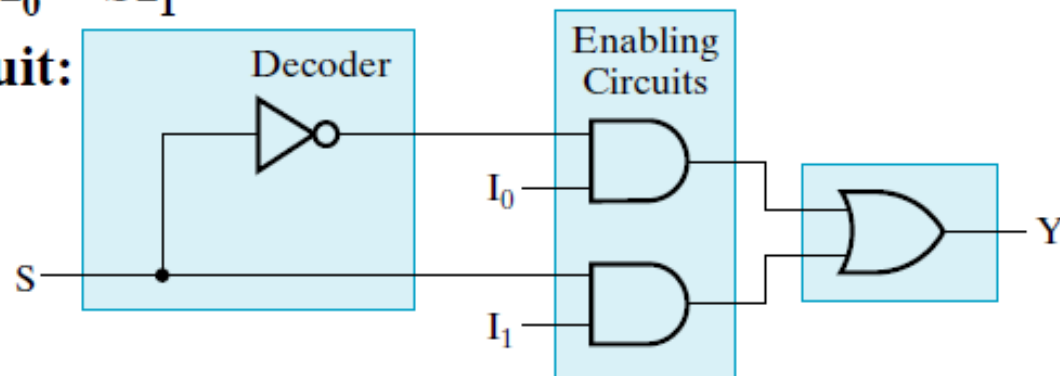

4 對 1 多工器

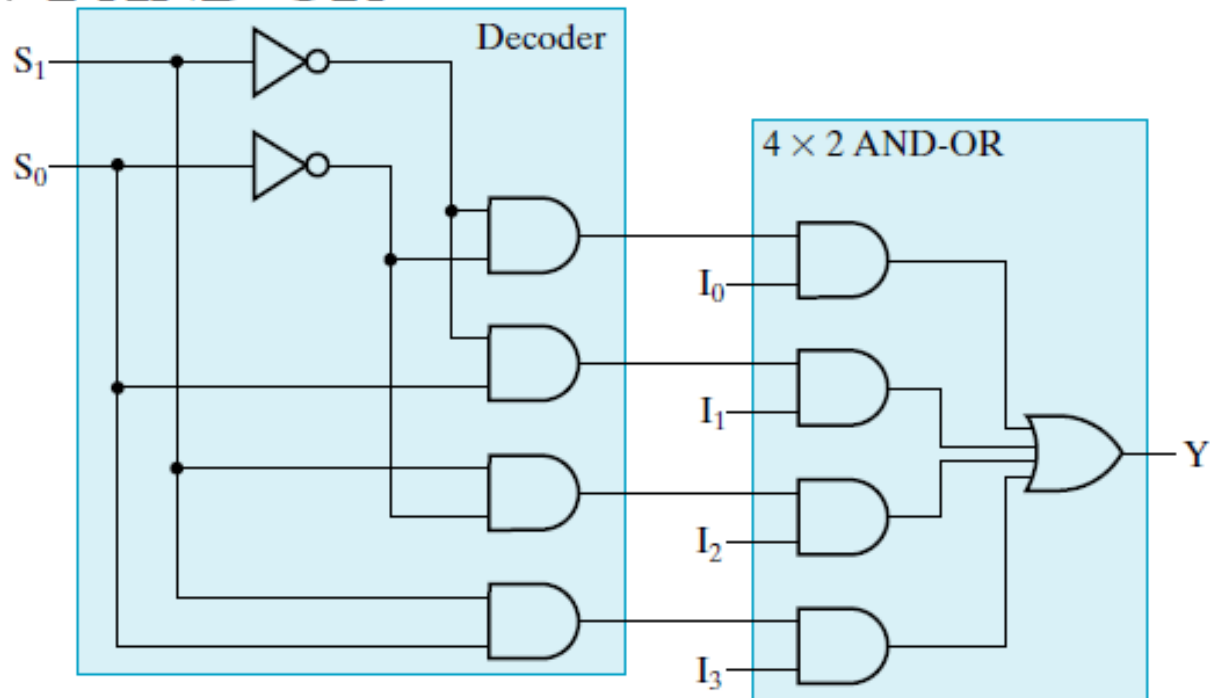Example: 4-to-1-line Multiplexer


- 2-to- 2^2 -line decoder
- $2^2 \times 2$ AND-OR



多工器的擴展

Multiplexer Width Expansion

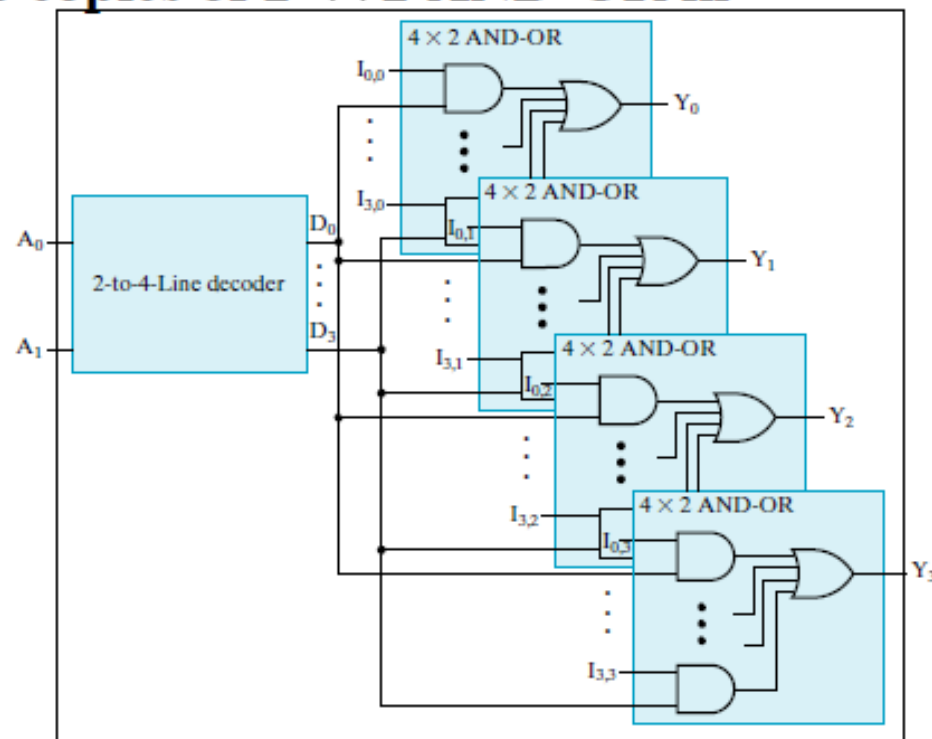
- Select “vectors of bits” instead of “bits”
- Use multiple copies of $2^n \times 2$ AND-OR in parallel
- Example:
4-to-1-line quad multiplexer



使用三態緩衝器實作

Other Selection Implementations

- Three-state logic in place of AND-OR

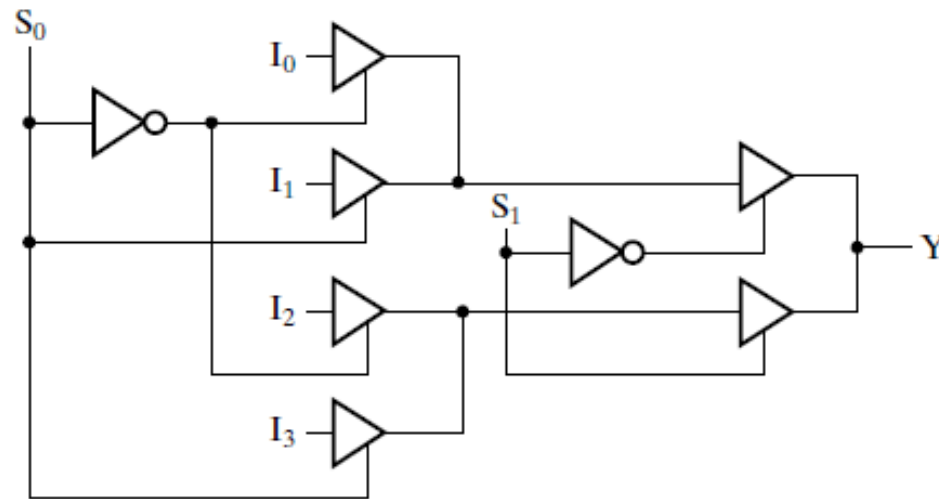

(b)

- Gate input cost = 14 compared to 22 (or 18) for gate implementation

授權限制

- 本投影片部份取材自邏輯與計算機設計 之投影片
 - 來源：<http://writphotec.com/mano4/>
 - 使用時請遵照下列條款

Terms of Use

- All (or portions) of this material © 2008 by Pearson Education, Inc.
- Permission is given to incorporate this material or adaptations thereof into classroom presentations and handouts to instructors in courses adopting the latest edition of Logic and Computer Design Fundamentals as the course textbook.
- These materials or adaptations thereof are not to be sold or otherwise offered for consideration.
- This Terms of Use slide or page is to be included within the original materials or any adaptations thereof.